

effects. A frequency-to-voltage converter can reconvert the pulse train to an analog voltage. The result is a cheap, compact circuit in which the duty cycle of the pulse train at  $F_{OUT}$  is directly proportional to the measured quantity. Alternatively, you can feed the pulse train into a counter to generate a digital signal. In this case, the gate signal of the counter determines the resolution of the system. For example, the gate interval must be at least equal to  $1024/(0.9 \times CLK_{IN})$  for a resolution of 10 bits.


A disadvantage of the circuit in Figure 1 is that the speed of the optocoupler determines the maximum frequency of  $F_{OUT}$ . Low-cost optocouplers have low switching speeds, and their high-speed counterparts are often expensive. Adding positive feedback to the light-sensitive base of the phototransistor greatly increases its switching speed (Figure 2). By adding one transistor, four resistors, and a capacitor, this circuit increases the maximum data-rate capability of the optocoupler by a factor of 10.

Another approach is to use a differential line driver (Figure 3). Adding the differential line driver increases the maximum frequency through the PS2502-2 optocoupler from 5 to 32 kHz. This approach ideally suits low-power applications for which the clock rate of the VFC is typically 32 kHz. At  $V_{DD} = 3V$ , the power dissipation of the VFC is typically 2.7 mW, and you can further reduce this number by gating off the  $CLK_{IN}$  input when the circuit is not monitoring  $V_{IN}$ . This action shuts down the VFC, and its power dissipation typically reduces to 0.09 mW. For a range of 0V to  $V_{DD}$  on  $V_{IN}$ , the corresponding output range of  $F_{OUT}$  is 3.2 to 28.8 kHz.

#### DIGITAL ISOLATION


For applications that require high-speed data transmission, you can use digital-isolation techniques. The digital isolator in Figure 4 combines high-speed CMOS and air-core-transformer technology, supports data rates from dc to 100 Mbps, and operates at low power. The device has a quiescent current of 0.6 mA and a dynamic current of less than 230  $\mu A$ /Mbps. The circuit clocks the VFC at its maximum frequency of 1

Figure 2

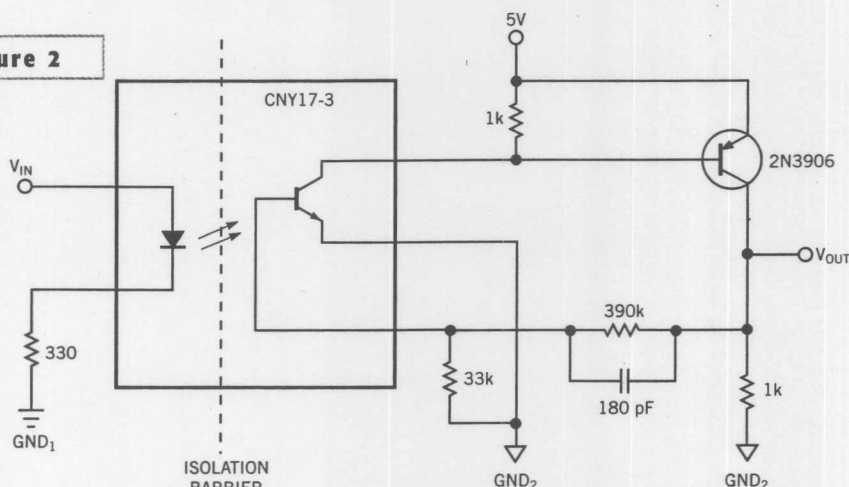


Adding positive feedback to the light-sensitive base of the phototransistor greatly increases its switching speed—in this case, to a maximum speed of 500 kHz.

Figure 3

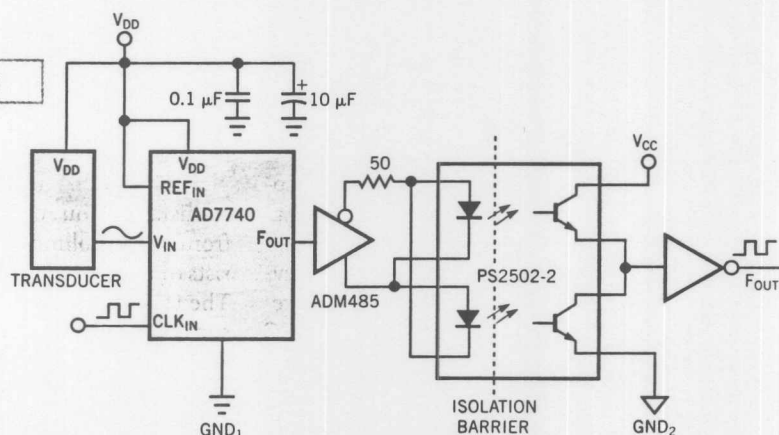

For low-power applications, adding a differential line driver increases the maximum frequency through the optocoupler from 5 to 32 kHz.

Figure 4

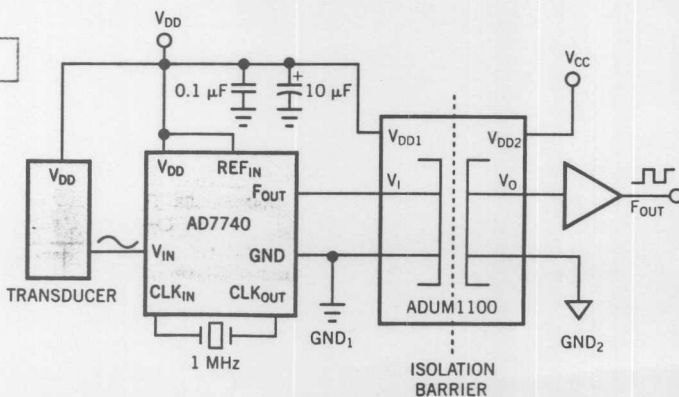

A digital isolator provides for high-speed data transmission—in this case, from dc to 100 Mbps.